

# THE *General Radio* EXPERIMENTER

VOLUME XXVI No. 5

OCTOBER, 1951

Copyright, 1951, General Radio Company, Cambridge, Mass., U. S. A.

ELECTRICAL MEASUREMENTS AND THEIR INDUSTRIAL APPLICATIONS

## A NEW PUSH-PULL AMPLIFIER CIRCUIT

● **AS ONE RESULT** of a continuing development program on audio-frequency instruments, a new audio power-amplifier circuit<sup>1,2</sup> that promises to be widely useful has been devised. In addition to being suitable for regular audio power amplifiers, this new circuit is particularly well adapted to amplifiers for constant-voltage audio distribution systems, to high-power modulators, to amplifiers for electronic musical instruments, and to audio amplifiers for industrial uses.

This new circuit permits one to obtain the high efficiency of Class AB<sub>1</sub> operation without switching transients, and this feature is obtained without the use of special components. The circuit also has important advantages for direct-coupled power amplifiers and for amplifiers operated Class A when very low distortion is required.

Because of the widespread interest already shown in this development, three practical high-power amplifiers using this new circuit with low-cost tubes will be described and component values will be given to aid the experimenter in making an initial setup. Before discussing these, however, the basic principle of the new circuit will be outlined briefly.


The basic circuit is shown in Figure 1. The output stage consists of two tubes connected in series across the d-c plate supply, and the load connects from the midpoint of this series connection to the plate supply.

The output tubes are driven in opposite phase by a phase-inverter stage. The important feature of this phase-inverter

<sup>1</sup>Arnold Peterson and Donald B. Sinclair, "A Single-Ended Push-Pull Audio Amplifier," 1951 I.R.E. National Convention, New York, N. Y., March 22, 1951, published in News Letter of I.R.E. Professional Group on Audio.

<sup>2</sup>Patent applied for.

Figure 1. The basic single-ended push-pull amplifier circuit, showing the series connected output tubes supplying a common load and driven by a cathode-follower phase inverter.

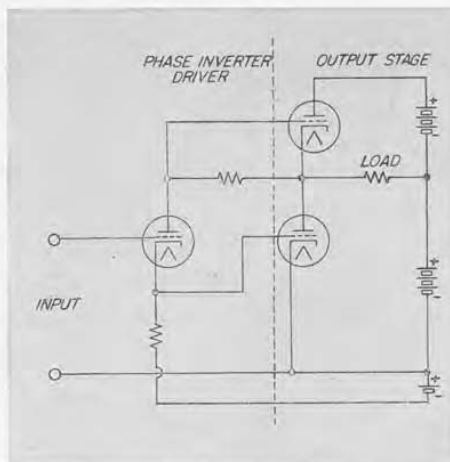

IET LABS, INC in the GenRad tradition

534 Main Street, Westbury, NY 11590

www.ietlabs.com

TEL: (516) 334-5959 • (800) 899-8438 • FAX: (516) 334-5988





pull amplifiers. They are often responsible for the objectionable harshness in so-called high-fidelity systems.

When beam-power tubes are used in the output, the two halves of the primary of the usual push-pull transformer can serve a useful purpose in this single-ended circuit by simplifying the problem of supplying the d-c screen-grid voltages to the two output tubes. How these can be used is shown in Figure 2. The output tubes are shown connected in series, as before, for the d-c supply. The screen-grid voltage for the upper tube is supplied through one primary winding from the plate supply. This upper screen-grid is by-passed to its cathode at the midpoint where the plate and output tubes are connected together. The other screen-grid is supplied through the other primary winding from the midpoint, and this lower screen-grid is by-passed to ground. The d-c screen-grid currents flow through the windings in the opposite sense, so that there is no net d-c flux from the screen-grid currents in the windings.

The transformer connections show that the two primary windings are connected in parallel for signal voltages. The screen-grid by-pass capacitors and the plate supply output capacitor make this parallel connection. These capacitors must provide a low-impedance path at the lowest signal frequency.


The circuit of Figure 2 also includes a feedback connection from the output stage to the first stage. Since the output is single-ended, feedback to a single-ended earlier stage is relatively simple. In the circuit shown, a fraction of the output voltage is applied directly to the cathode of the first stage as a voltage feedback.

The circuit of Figure 2 is arranged to operate the final stage Class AB<sub>1</sub>. Be-

cause this type of operation requires large driving voltages from the phase-inverter stage, the method of connection of this stage is different from that of Figure 1 in certain details. The d-c bias voltage for the upper output tube is obtained from only part of the phase-inverter plate load. The full signal voltage across the plate load, however, is applied to the upper tube through the coupling capacitor between the plate of the phase inverter and the grid of the upper tube.

The a-c plate voltage from plate to cathode of the phase inverter stage of Figure 1 is the sum of the a-c output voltage and the two a-c grid voltages produced across its load resistances. For a 50-watt amplifier using Type 1614 tubes, this a-c voltage is of the order of 500 volts peak. The d-c plate voltage required across this tube, then, must be greater than 500 volts in order to avoid serious non-linearity in the driver stage. If the experimenter has available a tube that can readily handle these voltages, the basic cathode-follower phase inverter of Figure 1 is recommended. In the particular circuit of Figure 2, a standard receiving type has been used within its rating of 500 volts by the circuit dodges shown. The resistance in the cathode is lower than necessary for full drive of the lower stage, so that the required voltage must be obtained from the previous amplifier stage. This lower resistance reduces the a-c voltage appearing from plate to cathode and makes possible the use of a Type 6S4 Triode within its 500-volt rating.

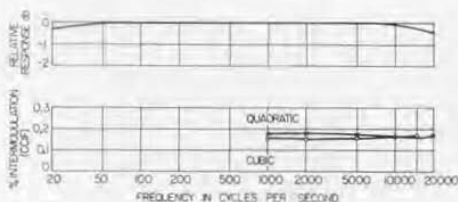The amplifier circuit of Figure 2 can be used with two Type 1614's in the output stage to yield 50 watts output. At this level the distortion can readily be held to less than 1% (total harmonic) for frequencies in the middle audio



range. By careful adjustment of balance and operating conditions, this distortion can be reduced even further.

The intermodulation results by the CCIF test<sup>4</sup> shown in Figure 3 demonstrate that the amplifier is operating correctly, with low distortion over the audio range. Measurements of intermodulation by the SMPTE method also showed satisfactorily low distortion. Tests at an equivalent 50-watt power level, using a low-frequency tone of 40 cps of four times the intensity of the high-frequency tone of 7000 cps, gave a total intermodulation of 1.6%, which is well below the 5% frequently used for rating high-quality systems.

Beyond the 50-watt limit, the output tubes are driven to the level where they draw grid current, which changes the operating conditions for the tubes. This change will give the results shown in the graphs, which were measured under steady state conditions. For dynamic conditions, such as occur with speech

and music signals, the distortion levels above 50 watts will be somewhat higher. This power level is obtained within the ICAS ratings of the Type 1614 and is the power available at the primary of the transformer. Because of the losses in the transformer, the power available at the secondary is reduced somewhat. When the General Radio TYPE 942-A Output Transformer<sup>5</sup> is used as specified, the reduction in available power is relatively small. The output transformer also limits the maximum low-frequency power obtainable from the amplifier. The TYPE 942-A Output Transformer<sup>5</sup> has been designed to handle a particularly high level of power, for its size, at low frequencies. The curve of Figure 4 shows its performance with the amplifier of Figure 2.

The element values given in Figure 2 have been determined to be suitable for an amplifier using four Type 1614's in

parallel. The element values given in Figure 2 have been determined to be suitable for an amplifier using four Type 1614's in

parallel. The element values given in Figure 2 have been determined to be suitable for an amplifier using four Type 1614's in

<sup>4</sup>A. P. G. Peterson, "An Audio-Frequency Signal Generator for Non-Linear Distortion Tests," *General Radio Experimenter*, August, 1950.

<sup>5</sup>To be described in next month's *Experimenter*.

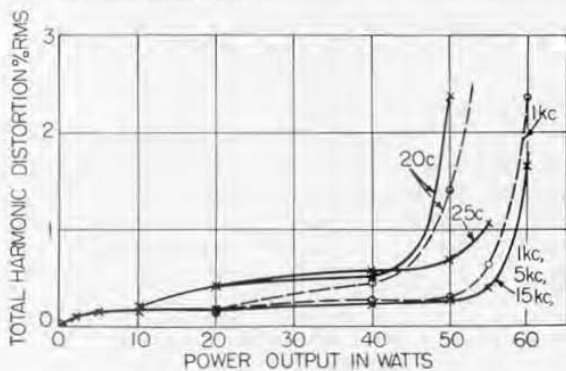


Figure 4. Harmonic distortion as a function of power delivered to the load for the circuit of Figure 2. All the curves except the dashed ones were taken with a 1500-ohm load across the primary. Since there was no essential difference in results at 1, 5, and 15 kc, only one curve is shown for these three frequencies. For frequencies above 50 cps, the results were also practically identical with the 1-kc curve. The dashed curves show the results with the load on the secondary of the transformer.







d-c plate currents is necessary here in order to avoid an unbalanced flux in the transformer.

Because of the way the screen-grid voltages must be supplied, the voltage drop in the two primary halves appears in the supply for the screen-grid of the upper output tube. There is no compensating drop in voltage for the screen-grid of the lower tube. In the circuit of Figure 6, the major part of this difference is taken care of by the use of different voltage-regulator tubes in the two screen-grid supplies. Otherwise, this circuit is essentially the same as that of Figure 2, and the performance is comparable as shown by Figure 7.

The circuit can be appreciably simplified if the full 50-watt power level is not required. A suitable circuit for an output power of 25 watts is shown in Figure 8.

The feedback used in these circuits is about 14 db. This amount is adequate to give a source impedance of about one-fifth the optimum load impedance, which is satisfactory for most applications. This source impedance can be reduced further by increasing the feedback. With the type of feedback used here, however, an increase in feedback usually results in a small decrease in available power, because of the power absorbed in the feedback circuit.

If the distortion from this amplifier is to be kept low, good quality resistors must be used in the feedback circuit. In

particular, it is recommended that the resistor from the primary of the transformer to the cathode of the first tube and the resistor to ground from the cathode of the first tube be wire-wound. Some composition resistors have an appreciable voltage coefficient, and, if they are used for the feedback circuit, they can contribute appreciable amounts of distortion.

For best operation at high audio frequencies, it is important to keep stray circuit capacitances as small as possible. Particular attention should be paid to the capacitance to ground of the circuit from the plate of the driver stage to the grid of the upper output tube. This capacitance, which shunts the phase-inverter plate-load impedance, is effectively multiplied by the gain of the output stage. For the present circuit this factor is about ten.

The circuits should be adjusted by observations using a high-resistance d-c voltmeter, a sinusoidal signal source, and a cathode-ray oscillograph. The bias adjustments should be made first to give about the values shown in the figures. Then a 1-kc signal should be applied and the signal balance adjustment should be made. Proper adjustment of this balance can be observed on the c-r-o at levels above 50 watts by noting the condition for equal clipping of the upper and lower peaks.

For best operation at low frequencies, the d-c currents in the two halves of the primary of the output transformer should be carefully balanced. This balance can usually be obtained by adjusting the grid biases. Occasionally some tube selection is desirable.

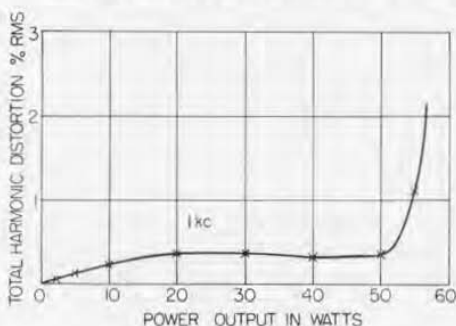


Figure 7. Harmonic distortion at 1 kc as a function of the power delivered to a 1500-ohm load across the primary for the d-c parallel connection of output tubes as shown in Figure 6.







## MISCELLANY

**CREDITS**—The single-ended push-pull amplifier described in this issue was originally developed by Dr. Donald B. Sinclair and Dr. Arnold P. G. Peterson. Credit is also due to Carlton A. Woodward, Jr., and William F. Byers for their helpful suggestions and to Mr. Woodward for his assistance in the experimental work.

**RECENT VISITORS** from other countries to our plant and laboratories include:

**From Denmark:**

DR. L. T. MUUS, Lecturer, Technical University of Copenhagen; JENS R. JENSEN, Associate Professor, Laboratory of Telegraphy and Telephony, Royal Danish Technical University, Copenhagen.

**From England:**

J. W. HARLING, Development Engineer, Standard Telephones & Cables, Ltd., London.

**From Venezuela:**

L. G. JIMINEZ, President, Intelec, S. A., Caracas.

**From Canada:**

D. T. REID, Sales Manager, Commercial Products Division, and T. V. SWEENEY, Project Controller, Commercial Products Division, Canadian Marconi Co., Ltd., Montreal, distributors of General Radio products in Canada; W. A. ANDERSON, Ryerson Institute of Technology, Toronto; J. H. DOBLE, Canadian General Electric Co., Ltd., Toronto.

**From Israel:**

JACOB ROSIN, Director, Electronic Equipment, Tel-Aviv.

**From Indonesia:**

E. TH. VERMAST, Manager, Radio and Electronic Department, Nelson and Brown Agencies, Ltd., Djakarta, who was accompanied by AD. AURIEMA, New York, export representative in Latin American countries for General Radio products.

---

***THE General Radio EXPERIMENTER is mailed without charge each month to engineers, scientists, technicians, and others interested in communication-frequency measurement and control problems. When sending requests for subscriptions and address-change notices, please supply the following information: name, company address, type of business company is engaged in, and title or position of individual.***

---

## GENERAL RADIO COMPANY

275 MASSACHUSETTS AVENUE

CAMBRIDGE 39

MASSACHUSETTS

TELEPHONE: TR owbridge 6-4400

## BRANCH ENGINEERING OFFICES

NEW YORK 6, NEW YORK  
90 WEST STREET  
TEL.—WOrth 2-5837

LOS ANGELES 38, CALIFORNIA  
1000 NORTH SEWARD STREET  
TEL.—HOLlywood 9-6201

CHICAGO 5, ILLINOIS  
920 SOUTH MICHIGAN AVENUE  
TEL.—WABash 2-3820

PRINTED  
IN  
U.S.A.

IET LABS, INC in the GenRad tradition

534 Main Street, Westbury, NY 11590

TEL: (516) 334-5959 • (800) 899-8438 • FAX: (516) 334-5988

www.ietlabs.com